

# DEPARTMENT OF INFORMATION TECHNOLOGY

## NATIONAL INSTITUTE OF TECHNOLOGY SRINAGAR

### Microprocessor Lab Assignment

**Note:**

- Use hardware description languages such as Verilog or VHDL to complete the following assignments.
- A maximum of two students are allowed to form a group for the assignment.
- However, if any of the students in the group is not able to explain the work done, he/she will get zero marks.

**Submission Timeline:**

**Part 1 and 2** - 14/11/2024 (group B) and 15/11/2024 (group A)

**Part 3:** Will be informed.

#### **Part 1:**

- 1) Design a 4-bit equality comparator circuit that has two 4-bit binary inputs (A and B) and outputs a logic-1 if both inputs are equal.
- 2) Design a 4-bit adder.
- 3) Design the circuits for multiplication.
- 4) Design the circuits for division.

#### **Part 2:**

- 1) Implement an Arithmetic Logic Unit (ALU).

Required: Develop an ALU that takes two 8-bit inputs A and B, and executes the following six instructions: **add, sub, and, or, xor, nor**.

The ALU generates an 8-bit output that we call 'Result' and an additional 1-bit flag 'Zero' that will be set to 'logic-1' if all the bits of 'Result' are 0.

Note: Draw a block diagram that will implement the ALU operations listed above.

### **Part 3:**

- 1) Design an in-order processor, in which the main execution unit, that is, ALU is at least able to perform functions listed in Part 2 of the assignment.