

Department of Information Technology
National Institute of Technology Srinagar

Hazratbal, Srinagar, Jammu and Kashmir - 190006, India.

ASSIGNMENT

Microprocessor Lab

Submitted by

KHUSHBOO

2022BITE002

Tavaheed Tariq

2022BITE008

B.TECH. IT(5th semester Section A)



Submit to

Dr. Janibul Bashir

Department of Information Technology
National Institute of Technology, Srinagar

AUTUMN 2024

ASSIGNMENT

Part 1:

1. Design a 4-bit equality comparator circuit that has two 4-bit binary inputs (A and B) and outputs a logic-1 if both inputs are equal.
2. Design a 4-bit adder.
3. Design the circuits for multiplication.
4. Design the circuits for division.

PART 1-1: Design a 4-bit equality comparator circuit that has two 4-bit binary inputs (A and B) and outputs a logic-1 if both inputs are equal.

```
library IEEE;
use IEEE.std_logic_1164.all;
entity comparator_VHDL is
port (
    A,B: in std_logic_vector(1 downto 0); -- two inputs for comparison
    A_less_B: out std_logic; -- '1' if A < B else '0'
    A_equal_B: out std_logic;-- '1' if A = B else '0'
    A_greater_B: out std_logic-- '1' if A > B else '0'
);
end comparator_VHDL;
architecture comparator_structural of comparator_VHDL is
    signal tmp1,tmp2,tmp3,tmp4,tmp5, tmp6, tmp7, tmp8: std_logic;
    -- temporary signals
begin
    -- A_equal_B combinational logic circuit
    tmp1 <= A(1) xnor B(1);
    tmp2 <= A(0) xnor B(0);
    A_equal_B <= tmp1 and tmp2;
    -- A_less_B combinational logic circuit
    tmp3 <= (not A(0)) and (not A(1)) and B(0);
    tmp4 <= (not A(1)) and B(1);
    tmp5 <= (not A(0)) and B(1) and B(0);
    A_less_B <= tmp3 or tmp4 or tmp5;
    -- A_greater_B combinational logic circuit
    tmp6 <= (not B(0)) and (not B(1)) and A(0);
    tmp7 <= (not B(1)) and A(1);
    tmp8 <= (not B(0)) and A(1) and A(0);
```

```
A_greater_B <= tmp6 or tmp7 or tmp8;
end comparator_structural;
```

```
--testbench
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.numeric_std.all;
ENTITY tb_comparator_VHDL IS
END tb_comparator_VHDL;

ARCHITECTURE behavior OF tb_comparator_VHDL IS

    -- Component Declaration for the comparator in VHDL

    COMPONENT comparator_VHDL
    PORT(
        A : IN  std_logic_vector(1 downto 0);
        B : IN  std_logic_vector(1 downto 0);
        A_less_B : OUT  std_logic;
        A_equal_B : OUT  std_logic;
        A_greater_B : OUT  std_logic
    );
    END COMPONENT;
--Inputs
signal A : std_logic_vector(1 downto 0) := (others => '0');
signal B : std_logic_vector(1 downto 0) := (others => '0');
--Outputs
signal A_less_B : std_logic;
signal A_equal_B : std_logic;
signal A_greater_B : std_logic;
BEGIN

    -- Instantiate the comparator in VHDL
    uut: comparator_VHDL PORT MAP (
        A => A,
        B => B,
        A_less_B => A_less_B,
        A_equal_B => A_equal_B,
        A_greater_B => A_greater_B
    );


    -- Stimulus process
    stim_proc: process
    begin
        -- create test cases for A_less_B
```

```

for i in 0 to 3 loop
    A <= std_logic_vector(to_unsigned(i,2));
    B <= std_logic_vector(to_unsigned(i+1,2));
    wait for 20 ns;
end loop;
-- create test cases for A_greater_B
for i in 0 to 3 loop
    A <= std_logic_vector(to_unsigned(i+1,2));
    B <= std_logic_vector(to_unsigned(i,2));
    wait for 20 ns;
end loop;
-- create test cases for A_equal_B
for i in 0 to 3 loop
    A <= std_logic_vector(to_unsigned(i,2));
    B <= std_logic_vector(to_unsigned(i,2));
    wait for 20 ns;
end loop;
wait;
end process;

END;

```

 

Steps to Simulate VHDL Code for Comparator Circuit

1. Compile the VHDL file for the comparator circuit:

```
ghdl -a comparator_VHDL.vhd
```

2. Compile the VHDL file for the comparator testbench:

```
ghdl -a tb_comparator_VHDL
```

3. Elaborate the Testbench

```
ghdl -e tb_comparator_VHDL
```

4. Run the Simulation

```
ghdl -r tb_comparator_VHDL --vcd=tb_comparator_VHDL.vcd
```

5. View the Waveform

```
gtkwave tb_comparator_VHDL.vcd
```

PART 1-2: Design a 4-bit adder.

```
-- FULL ADDER
library ieee;
use ieee.std_logic_1164.all;

entity Full_Adder is
    port(
        X, Y, Cin : in std_logic;
        Sum, Cout : out std_logic
    );
end Full_Adder;

architecture bhv of Full_Adder is
begin
    Sum <= (X xor Y) xor Cin;
    Cout <= (X and Y) or (Cin and (X xor Y));
end bhv;

-- 4-BIT ADDER
```

```

library ieee;
use ieee.std_logic_1164.all;

entity adder is
    port(
        A, B : in std_logic_vector(3 downto 0);
        R    : out std_logic_vector(3 downto 0);
        Cout : out std_logic
    );
end adder;

architecture struct of adder is
    component Full_Adder is
        port(
            X, Y, Cin : in std_logic;
            Sum, Cout : out std_logic
        );
    end component;

    signal C1, C2, C3, C4: std_logic;

begin
    FA0: Full_Adder port map(A(0), B(0), '0', R(0), C1); -- Least significant
    FA1: Full_Adder port map(A(1), B(1), C1, R(1), C2);
    FA2: Full_Adder port map(A(2), B(2), C2, R(2), C3);
    FA3: Full_Adder port map(A(3), B(3), C3, R(3), C4); -- Most significant
    Cout <= C4; -- Final carry-out
end struct;

```

```

--tb
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity adder_tb is
end adder_tb;

architecture behavior of adder_tb is
    -- Signal declarations for inputs and outputs
    signal a, b : std_logic_vector(3 downto 0);
    signal r    : std_logic_vector(3 downto 0);
    signal cout : std_logic;

    -- Component declaration
    component adder is

```

```

        port(
            A, B : in std_logic_vector(3 downto 0);
            R     : out std_logic_vector(3 downto 0);
            Cout  : out std_logic
        );
    end component;
begin
    -- Instantiate the adder
    uut: adder
        port map(
            A => a,      -- Match input A
            B => b,      -- Match input B
            R => r,      -- Match output R
            Cout => cout -- Match output Cout
        );


    -- Test process
    stim_proc: process
    begin
        -- Test case 1
        a <= "0001"; b <= "0010";
        wait for 10 ns;

        -- Test case 2
        a <= "0101"; b <= "1011";
        wait for 10 ns;

        -- Test case 3
        a <= "1111"; b <= "0001";
        wait for 10 ns;

        -- End of simulation
        wait;
    end process;
end behavior;

```

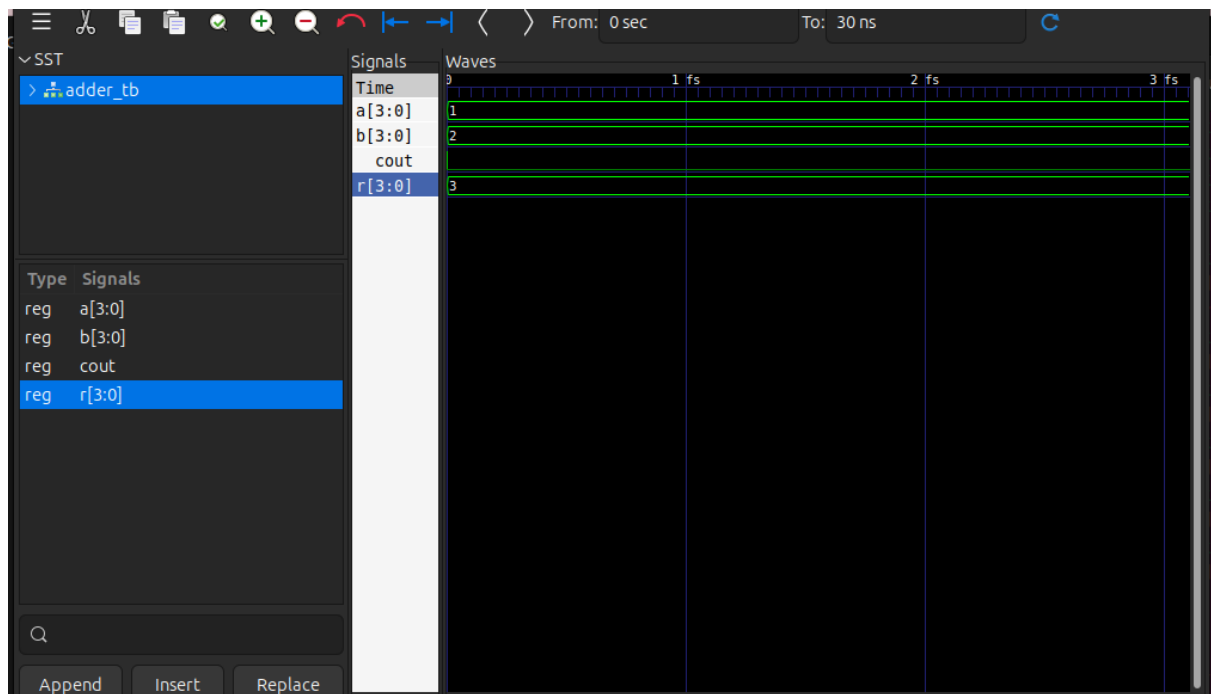

PART 1-3: Design the circuits for multiplication.

SIGNED MULTIPLIER

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity signed_multiplier is
    port (
        a, b : in signed(7 downto 0);
        result : out signed(15 downto 0)
    );
end entity signed_multiplier;

architecture rtl of signed_multiplier is
begin
    process(a, b)
    begin
        result <= resize(a * b, 16);
    end process;
end architecture rtl;
```

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
```



```

entity tb_signed_multiplier is
end entity tb_signed_multiplier;

architecture tb of tb_signed_multiplier is
    component signed_multiplier
        port (
            a, b : in signed(7 downto 0);
            result : out signed(15 downto 0)
        );
    end component;

    signal a, b : signed(7 downto 0);
    signal result : signed(15 downto 0);
begin
    dut : signed_multiplier
        port map (
            a => a,
            b => b,
            result => result
        );


    process
    begin
        -- Positive numbers
        a <= "00001010"; -- 10
        b <= "00000110"; -- 6
        wait for 10 ns;
        assert result = "00000000000111100" report "Test failed for 10 * 6";

        -- Negative numbers
        a <= "11110110"; -- -10
        b <= "11111010"; -- -6
        wait for 10 ns;
        assert result = "00000000000111100" report "Test failed for -10 * -6";

        -- Mixed signs
        a <= "00001010"; -- 10
        b <= "11111010"; -- -6
        wait for 10 ns;
        assert result = "1111111111000100" report "Test failed for 10 * -6";

        wait;
    end process;
end architecture tb;

```

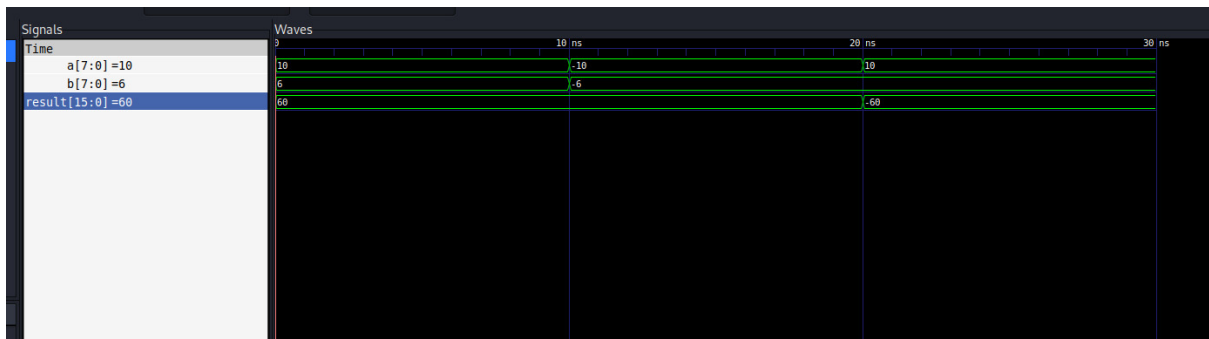

UNSIGNED MULTIPLIER

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity unsigned_multiplier is
    port (
        a, b : in unsigned(7 downto 0);
        result : out unsigned(15 downto 0)
    );
end entity unsigned_multiplier;

architecture rtl of unsigned_multiplier is
begin
    process(a, b)
    begin
        result <= a * b;
    end process;
end architecture rtl;
```

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity tb_unsigned_multiplier is
end entity tb_unsigned_multiplier;

architecture tb of tb_unsigned_multiplier is
    component unsigned_multiplier
        port (
            a, b : in unsigned(7 downto 0);
            result : out unsigned(15 downto 0)
        );
    end component;
```

```

    );
end component;

signal a, b : unsigned(7 downto 0);
signal result : unsigned(15 downto 0);
begin
    DUT : unsigned_multiplier
        port map (
            a => a,
            b => b,
            result => result
        );


    process
    begin
        a <= "00001010"; -- 10
        b <= "00000011"; -- 3
        wait for 10 ns;
        assert result = "00000000000011110" -- 30
            report "Test failed for 10 * 3" severity error;

        a <= "11111111"; -- 255
        b <= "00000001"; -- 1
        wait for 10 ns;
        assert result = "0000000011111111" -- 255
            report "Test failed for 255 * 1" severity error;

        a <= "00001111"; -- 15
        b <= "00001111"; -- 15
        wait for 10 ns;
        assert result = "0000000011100001" -- 225
            report "Test failed for 15 * 15" severity error;

        wait;
    end process;
end architecture tb;

```

 

PART 1-4: Design the circuits for division.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity division is
    port (
        a    : in integer range 0 to 255; -- Dividend
        b    : in integer range 1 to 17;  -- Divisor (range starts from 1)
        quo : out integer range 0 to 255 -- Quotient
    );
end entity division;

architecture structure of division is
begin
    process(a, b)
    begin
        -- Perform division and handle edge cases
        if b /= 0 then
            quo <= a / b; -- Calculate quotient
        else
            quo <= 0;      -- Default output when divisor is zero
        end if;
    end process;
end architecture structure;
```

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity division_tb is
end entity division_tb;

architecture behavior of division_tb is

    -- Component declaration for the unit under test (UUT)
    component division is
        port (
            a    : in integer range 0 to 255; -- Dividend
            b    : in integer range 1 to 17;  -- Divisor
            quo : out integer range 0 to 255 -- Quotient
        );
    end component;
```

```

    );
end component;

-- Signals to connect to the UUT
signal a_tb    : integer range 0 to 255 := 0;
signal b_tb    : integer range 1 to 17 := 1;
signal quo_tb  : integer range 0 to 255;

begin

    -- Instantiate the Unit Under Test (UUT)
    uut: division
        port map (
            a    => a_tb,
            b    => b_tb,
            quo => quo_tb
        );

    -- Stimulus process
    stimulus: process
    begin
        -- Test 1: A = 100, B = 5
        a_tb <= 100;
        b_tb <= 5;
        wait for 10 ns;

        -- Test 2: A = 255, B = 17
        a_tb <= 255;
        b_tb <= 17;
        wait for 10 ns;

        -- Test 3: A = 40, B = 8
        a_tb <= 40;
        b_tb <= 8;
        wait for 10 ns;

        -- Test 4: A = 7, B = 1
        a_tb <= 7;
        b_tb <= 1;
        wait for 10 ns;

        -- Test 5: A = 50, B = 3
        a_tb <= 50;
        b_tb <= 3;
        wait for 10 ns;
    end
end


```

```

-- End simulation
wait;
end process;

end architecture behavior;

```

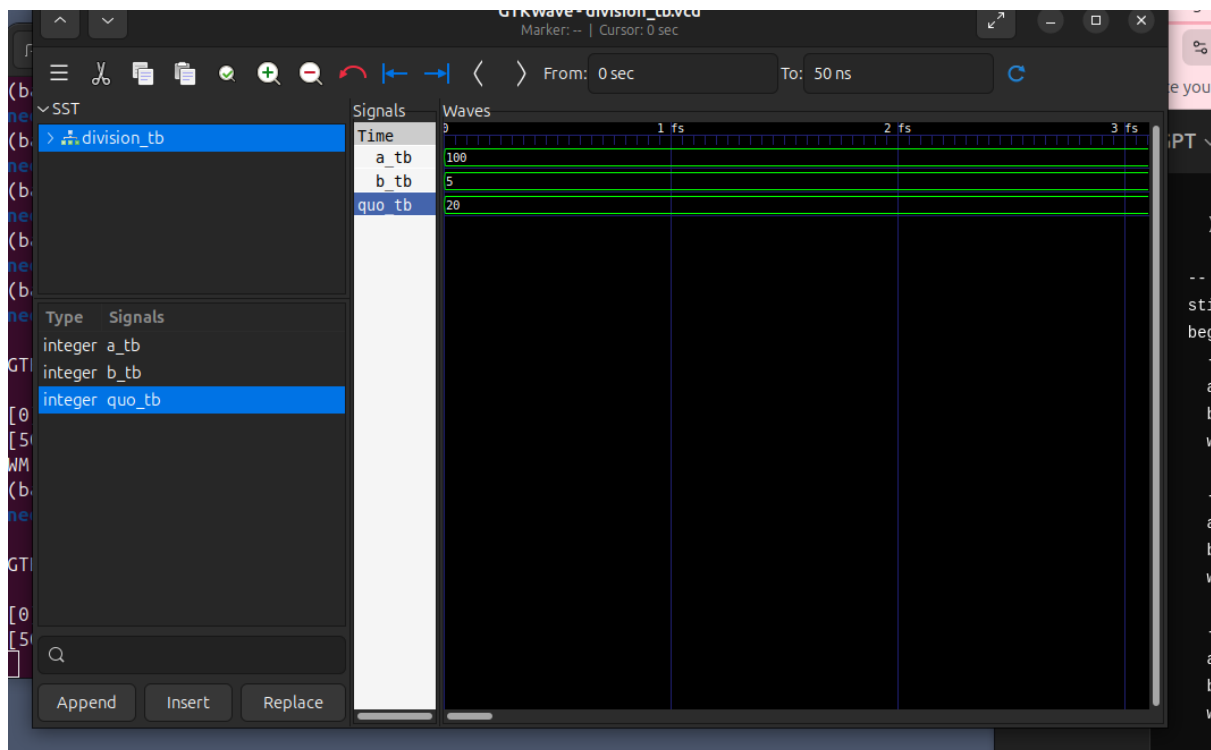

Part 2:

1. Implement an Arithmetic Logic Unit (ALU).
 Required: Develop an ALU that takes two 8-bit inputs A and B, and executes the following six instructions: add, sub, and, or, xor, nor.
 The ALU generates an 8-bit output that we call 'Result' and an additional 1-bit flag 'Zero' that will be set to 'logic-1' if all the bits of 'Result' are 0.
 Note: Draw a block diagram that will implement the ALU operations listed above.

PART 2: IMPLEMENT AN ALU

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use work.CustomALU_pkg.ALL;

```

```

entity ALU is
    Port (
        A : in STD_LOGIC_VECTOR (7 downto 0); -- 8-bit input A
        B : in STD_LOGIC_VECTOR (7 downto 0); -- 8-bit input B
        sel : in STD_LOGIC_VECTOR (2 downto 0); -- 3-bit select input
        Result : out STD_LOGIC_VECTOR (7 downto 0); -- 8-bit output Result
        Zero : out STD_LOGIC -- Zero flag
    );
end ALU;

```

architecture Behavioral of ALU is

begin

 process(A, B, sel)

 variable temp_result : STD_LOGIC_VECTOR (7 downto 0);

 begin

 case sel is

 when "000" => -- ADD

 temp_result := add_8bit(A, B);

 when "001" => -- SUBTRACT

 temp_result := sub_8bit(A, B);

 when "010" => -- AND

 temp_result := and_8bit(A, B);

 when "011" => -- OR

 temp_result := or_8bit(A, B);

 when "100" => -- XOR

 temp_result := xor_8bit(A, B);

 when "101" => -- NOR

 temp_result := nor_8bit(A, B);

 when others =>

 temp_result := (others => '0'); -- Default case

 end case;

 Result <= temp_result; -- Assign result to output

 -- Set the Zero flag

 if temp_result = "00000000" then

 Zero <= '1';

 else

 Zero <= '0';

 end if;

 end process;

end Behavioral;

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

```

use IEEE.NUMERIC_STD.ALL;
use work.CustomALU_pkg.ALL;

entity ALU_tb is
end ALU_tb;

architecture Behavioral of ALU_tb is
    -- Component Declaration
    component ALU
        Port (
            A : in STD_LOGIC_VECTOR (7 downto 0);
            B : in STD_LOGIC_VECTOR (7 downto 0);
            sel : in STD_LOGIC_VECTOR (2 downto 0);
            Result : out STD_LOGIC_VECTOR (7 downto 0);
            Zero : out STD_LOGIC
        );
    end component;

    -- Test Signals
    signal A_tb      : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');
    signal B_tb      : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');
    signal sel_tb     : STD_LOGIC_VECTOR (2 downto 0) := (others => '0');
    signal Result_tb  : STD_LOGIC_VECTOR (7 downto 0);
    signal Zero_tb    : STD_LOGIC;

    -- Helper procedure for printing test results
    procedure print_test_case(
        test_name: string;
        A, B: STD_LOGIC_VECTOR(7 downto 0);
        sel: STD_LOGIC_VECTOR(2 downto 0);
        result: STD_LOGIC_VECTOR(7 downto 0)) is
    begin
        report "Test: " & test_name &
            " | A=" & integer'image(to_integer(unsigned(A))) &
            " | B=" & integer'image(to_integer(unsigned(B))) &
            " | Result=" & integer'image(to_integer(unsigned(result)))
    end procedure;

begin
    -- Unit Under Test (UUT)
    UUT: ALU port map (
        A => A_tb,
        B => B_tb,
        sel => sel_tb,
        Result => Result_tb,

```



```

        Zero => Zero_tb
    );

    -- Stimulus Process
    stim_proc: process
    begin
        -- Wait for 10ns for global reset
        wait for 10 ns;

        -- Test Case 1: Addition (000)
        A_tb <= "00000101"; -- 5
        B_tb <= "00000011"; -- 3
        sel_tb <= "000";      -- ADD
        wait for 10 ns;
        print_test_case("Addition", A_tb, B_tb, sel_tb, Result_tb);
        wait for 3 fs;

        -- Test Case 2: Subtraction (001)
        A_tb <= "00001000"; -- 8
        B_tb <= "00000011"; -- 3
        sel_tb <= "001";      -- SUB
        wait for 10 ns;
        print_test_case("Subtraction", A_tb, B_tb, sel_tb, Result_tb);
        wait for 3 fs;

        -- Test Case 3: AND (010)
        A_tb <= "11110000";
        B_tb <= "00001111";
        sel_tb <= "010";      -- AND
        wait for 10 ns;
        print_test_case("AND", A_tb, B_tb, sel_tb, Result_tb);
        wait for 3 fs;

        -- Test Case 4: OR (011)
        A_tb <= "11110000";
        B_tb <= "00001111";
        sel_tb <= "011";      -- OR
        wait for 10 ns;
        print_test_case("OR", A_tb, B_tb, sel_tb, Result_tb);
        wait for 3 fs;

        -- Test Case 5: XOR (100)
        A_tb <= "11110000";
        B_tb <= "00001111";
        sel_tb <= "100";      -- XOR
    end
end

```

```

wait for 10 ns;
print_test_case("XOR", A_tb, B_tb, sel_tb, Result_tb);
wait for 3 fs;

-- Test Case 6: NOR (101)
A_tb <= "11110000";
B_tb <= "00001111";
sel_tb <= "101";      -- NOR
wait for 10 ns;
print_test_case("NOR", A_tb, B_tb, sel_tb, Result_tb);
wait for 3 fs;


-- Test Case 7: Zero flag test
A_tb <= "00000000";
B_tb <= "00000000";
sel_tb <= "000";      -- ADD
wait for 10 ns;
print_test_case("Zero Flag", A_tb, B_tb, sel_tb, Result_tb);
wait for 3 fs;


-- Test Case 8: Carry operation
A_tb <= "11111111";
B_tb <= "11111111";
sel_tb <= "111";      -- Carry operation
wait for 10 ns;
print_test_case("Carry Op", A_tb, B_tb, sel_tb, Result_tb);
wait for 3 fs;

-- End simulation
report "Simulation completed successfully";
wait;
end process;

end Behavioral;

```

 

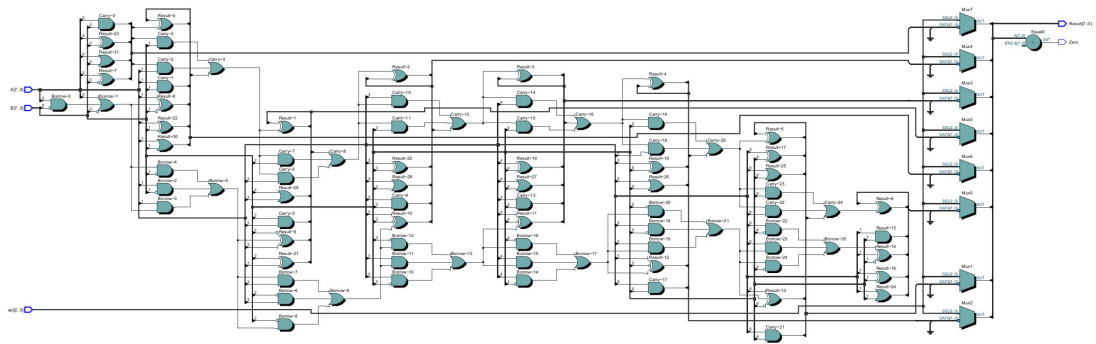

Part 3:

1. Design an in-order processor, in which the main execution unit , that is , ALU is at least able to perform functions listed in Part 2 of the assignment

PART 3: INORDER PROCESSOR

Directory structure

```
inorder_processor/  
├── src/  
│   ├── ALU.vhd  
│   ├── CustomALU_pkg.vhd  
│   ├── DataMem.vhd  
│   ├── InstrMem.vhd  
│   ├── Processor.vhd  
│   └── Top.vhd  
├── tb/  
│   ├── ALU_tb.vhd  
│   ├── Processor_tb.vhd  
│   └── Top_tb.vhd  
├── work/  
│   ├── processor_tb.vcd  
│   ├── top_tb.vcd  
│   ├── processor_wave.gtkw  
│   └── top_wave.gtkw  
├── simulate.sh  
└── view_waves.sh
```

ALU.vhd

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use work.CustomALU_pkg.ALL;  
  
entity ALU is  
    Port (  
        A : in STD_LOGIC_VECTOR (7 downto 0); -- 8-bit input A  
        B : in STD_LOGIC_VECTOR (7 downto 0); -- 8-bit input B  
        sel : in STD_LOGIC_VECTOR (2 downto 0); -- 3-bit select input  
        Result : out STD_LOGIC_VECTOR (7 downto 0); -- 8-bit output Result  
        Zero : out STD_LOGIC -- Zero flag  
    );  
end ALU;
```

```

architecture Behavioral of ALU is
begin
    process(A, B, sel)
        variable temp_result : STD_LOGIC_VECTOR (7 downto 0);
        begin
            case sel is
                when "000" => -- ADD
                    temp_result := add_8bit(A, B);
                when "001" => -- SUBTRACT
                    temp_result := sub_8bit(A, B);
                when "010" => -- AND
                    temp_result := and_8bit(A, B);
                when "011" => -- OR
                    temp_result := or_8bit(A, B);
                when "100" => -- XOR
                    temp_result := xor_8bit(A, B);
                when "101" => -- NOR
                    temp_result := nor_8bit(A, B);
                when others =>
                    temp_result := (others => '0'); -- Default case
            end case;

            Result <= temp_result; -- Assign result to output

            -- Set the Zero flag
            if temp_result = "00000000" then
                Zero <= '1';
            else
                Zero <= '0';
            end if;
        end process;
    end Behavioral;

```

CustomALU_Pkg.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

package CustomALU_Pkg is
    function add_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(7 downto 0);
    function sub_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(7 downto 0);
    function and_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(7 downto 0);
    function or_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(7 downto 0);
    function xor_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(7 downto 0);
    function nor_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(7 downto 0);
end package CustomALU_Pkg;

```

```

function nor_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC;
end CustomALU_Pkg;

package body CustomALU_Pkg is
  -- Addition Function
  function add_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(8 downto 0) is
    variable Result: STD_LOGIC_VECTOR(7 downto 0);
    variable Carry: STD_LOGIC_VECTOR(8 downto 0); -- One extra bit for carry
  begin
    Carry(0) := '0'; -- Initial carry is 0

    for i in 0 to 7 loop
      Result(i) := A(i) xor B(i) xor Carry(i);
      Carry(i+1) := (A(i) and B(i)) or (A(i) and Carry(i)) or (B(i) and Carry(i));
    end loop;

    return Result;
  end function;

  -- Subtraction Function
  function sub_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(8 downto 0) is
    variable Result: STD_LOGIC_VECTOR(7 downto 0);
    variable Borrow: STD_LOGIC_VECTOR(8 downto 0); -- One extra bit for borrow
    variable B_comp: STD_LOGIC_VECTOR(7 downto 0); -- Two's complement of B
  begin
    -- Create two's complement of B
    B_comp := not B;
    Borrow(0) := '1'; -- Add 1 for two's complement

    for i in 0 to 7 loop
      Result(i) := A(i) xor B_comp(i) xor Borrow(i);
      Borrow(i+1) := (A(i) and B_comp(i)) or (A(i) and Borrow(i)) or (B_comp(i) and Borrow(i));
    end loop;

    return Result;
  end function;

  -- Bitwise AND (no changes needed)
  function and_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(7 downto 0) is
    variable Result: STD_LOGIC_VECTOR(7 downto 0);
  begin
    for i in 7 downto 0 loop
      Result(i) := A(i) and B(i);
    end loop;
    return Result;
  end function;
end CustomALU_Pkg;

```

```

end function;

-- Bitwise OR (no changes needed)
function or_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(7 downto 0)
    variable Result: STD_LOGIC_VECTOR(7 downto 0);
begin
    for i in 7 downto 0 loop
        Result(i) := A(i) or B(i);
    end loop;
    return Result;
end function;

-- Bitwise XOR (no changes needed)
function xor_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(7 downto 0)
    variable Result: STD_LOGIC_VECTOR(7 downto 0);
begin
    for i in 7 downto 0 loop
        Result(i) := A(i) xor B(i);
    end loop;
    return Result;
end function;

-- Bitwise NOR (no changes needed)
function nor_8bit(A, B: STD_LOGIC_VECTOR(7 downto 0)) return STD_LOGIC_VECTOR(7 downto 0)
    variable Result: STD_LOGIC_VECTOR(7 downto 0);
begin
    for i in 7 downto 0 loop
        Result(i) := not (A(i) or B(i));
    end loop;
    return Result;
end function;
end CustomALU_Pkg;

```

DataMem.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity DataMem is
    Port (
        clk : in STD_LOGIC;
        addr : in STD_LOGIC_VECTOR(7 downto 0);
        data_in : in STD_LOGIC_VECTOR(7 downto 0);
        data_out : out STD_LOGIC_VECTOR(7 downto 0);
    );
end entity DataMem;

```

```

        wr_en : in STD_LOGIC
    );
end DataMem;

architecture Behavioral of DataMem is
    type mem_type is array (0 to 255) of STD_LOGIC_VECTOR(7 downto 0);
    signal memory : mem_type := (others => (others => '0'));
begin
    process(clk)
    begin
        if rising_edge(clk) then
            if wr_en = '1' then
                memory(to_integer(unsigned(addr))) <= data_in;
            end if;
            data_out <= memory(to_integer(unsigned(addr)));
        end if;
    end process;
end Behavioral;

```

InstrMem.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity InstrMem is
    Port (
        clk : in STD_LOGIC;
        addr : in STD_LOGIC_VECTOR(7 downto 0);
        instr : out STD_LOGIC_VECTOR(31 downto 0)
    );
end InstrMem;

architecture Behavioral of InstrMem is
    type mem_type is array (0 to 255) of STD_LOGIC_VECTOR(31 downto 0);
    signal memory : mem_type := (
        -- Example program
        0 => "0000000000000001100000001000000000", -- ADD R3, R2
        1 => "0010000000000010000000001100000000", -- SUB R4, R3
        2 => "0100000000000010100000010000000000", -- AND R5, R4
        3 => "0110000000000011000000010100000000", -- OR R6, R5
        4 => "1000000000000011100000011000000000", -- XOR R7, R6
        5 => "1010000000000100000000011100000000", -- NOR R8, R7
        others => (others => '0')
    );
end Behavioral;

```



```

begin
    process(clk)
    begin
        if rising_edge(clk) then
            instr <= memory(to_integer(unsigned(addr)));
        end if;
    end process;
end Behavioral;

```

Processor.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity Processor is
    Port (
        clk : in STD_LOGIC;
        reset : in STD_LOGIC;

        -- Instruction Memory Interface
        instr_addr : out STD_LOGIC_VECTOR (7 downto 0);
        instr : in STD_LOGIC_VECTOR (31 downto 0);

        -- Data Memory Interface
        data_addr : out STD_LOGIC_VECTOR (7 downto 0);
        data_in : out STD_LOGIC_VECTOR (7 downto 0);
        data_out : in STD_LOGIC_VECTOR (7 downto 0);
        data_wr : out STD_LOGIC
    );
end Processor;

architecture Behavioral of Processor is
    -- Components
    component ALU
        Port (
            A : in STD_LOGIC_VECTOR (7 downto 0);
            B : in STD_LOGIC_VECTOR (7 downto 0);
            sel : in STD_LOGIC_VECTOR (2 downto 0);
            Result : out STD_LOGIC_VECTOR (7 downto 0);
            Zero : out STD_LOGIC
        );
    end component;

    -- Processor Signals

```

```

signal PC : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');
signal Inst_Reg : STD_LOGIC_VECTOR (31 downto 0);
signal Reg_A, Reg_B : STD_LOGIC_VECTOR (7 downto 0);
signal ALU_Res : STD_LOGIC_VECTOR (7 downto 0);
signal ALU_Ctrl : STD_LOGIC_VECTOR (2 downto 0);
signal Zero_Flag : STD_LOGIC;

begin
  -- Instruction Fetch
  instr_addr <= PC;
  Inst_Reg <= instr;

  -- Instruction Decode
  process(Inst_Reg)
  begin
    case Inst_Reg(31 downto 29) is
      when "000" => ALU_Ctrl <= "000"; -- ADD
      when "001" => ALU_Ctrl <= "001"; -- SUB
      when "010" => ALU_Ctrl <= "010"; -- AND
      when "011" => ALU_Ctrl <= "011"; -- OR
      when "100" => ALU_Ctrl <= "100"; -- XOR
      when "101" => ALU_Ctrl <= "101"; -- NOR
      when others => ALU_Ctrl <= "111"; -- Invalid
    end case;

    Reg_A <= Inst_Reg(23 downto 16);
    Reg_B <= Inst_Reg(15 downto 8);
  end process;

  -- ALU Execution
  ALU_Unit: ALU
    port map (
      A => Reg_A,
      B => Reg_B,
      sel => ALU_Ctrl,
      Result => ALU_Res,
      Zero => Zero_Flag
    );

  -- Memory Access
  data_addr <= ALU_Res(7 downto 0);
  data_in <= Reg_B;
  data_wr <= '1' when ALU_Ctrl = "000" else '0'; -- Write for ADD only

  -- Program Counter Update

```

```

process(clk, reset)
begin
    if reset = '1' then
        PC <= (others => '0');
    elsif rising_edge(clk) then
        PC <= std_logic_vector(unsigned(PC) + 1);
    end if;
end process;

end Behavioral;

```

Top.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Top is
    Port (
        clk : in STD_LOGIC;
        reset : in STD_LOGIC
    );
end Top;

architecture Behavioral of Top is
    -- Component declarations
    component Processor is
        Port (
            clk : in STD_LOGIC;
            reset : in STD_LOGIC;
            instr_addr : out STD_LOGIC_VECTOR(7 downto 0);
            instr : in STD_LOGIC_VECTOR(31 downto 0);
            data_addr : out STD_LOGIC_VECTOR(7 downto 0);
            data_in : out STD_LOGIC_VECTOR(7 downto 0);
            data_out : in STD_LOGIC_VECTOR(7 downto 0);
            data_wr : out STD_LOGIC
        );
    end component;

    component InstrMem is
        Port (
            clk : in STD_LOGIC;
            addr : in STD_LOGIC_VECTOR(7 downto 0);
            instr : out STD_LOGIC_VECTOR(31 downto 0)
        );
    end component;

```

```

component DataMem is
    Port (
        clk : in STD_LOGIC;
        addr : in STD_LOGIC_VECTOR(7 downto 0);
        data_in : in STD_LOGIC_VECTOR(7 downto 0);
        data_out : out STD_LOGIC_VECTOR(7 downto 0);
        wr_en : in STD_LOGIC
    );
end component;

-- Internal signals
signal instr_addr : STD_LOGIC_VECTOR(7 downto 0);
signal instruction : STD_LOGIC_VECTOR(31 downto 0);
signal data_addr : STD_LOGIC_VECTOR(7 downto 0);
signal data_to_mem : STD_LOGIC_VECTOR(7 downto 0);
signal data_from_mem : STD_LOGIC_VECTOR(7 downto 0);
signal data_wr : STD_LOGIC;

begin
    -- Processor instantiation
    proc: Processor
        port map (
            clk => clk,
            reset => reset,
            instr_addr => instr_addr,
            instr => instruction,
            data_addr => data_addr,
            data_in => data_to_mem,
            data_out => data_from_mem,
            data_wr => data_wr
        );

    -- Instruction Memory instantiation
    imem: InstrMem
        port map (
            clk => clk,
            addr => instr_addr,
            instr => instruction
        );

    -- Data Memory instantiation
    dmem: DataMem
        port map (
            clk => clk,

```

```

        addr => data_addr,
        data_in => data_to_mem,
        data_out => data_from_mem,
        wr_en => data_wr
    );

end Behavioral;

```

ALU_tb.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use work.CustomALU_pkg.ALL;

entity ALU_tb is
end ALU_tb;

architecture Behavioral of ALU_tb is
    -- Component Declaration
    component ALU
        Port (
            A : in STD_LOGIC_VECTOR (7 downto 0);
            B : in STD_LOGIC_VECTOR (7 downto 0);
            sel : in STD_LOGIC_VECTOR (2 downto 0);
            Result : out STD_LOGIC_VECTOR (7 downto 0);
            Zero : out STD_LOGIC
        );
    end component;

    -- Test Signals
    signal A_tb      : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');
    signal B_tb      : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');
    signal sel_tb    : STD_LOGIC_VECTOR (2 downto 0) := (others => '0');
    signal Result_tb : STD_LOGIC_VECTOR (7 downto 0);
    signal Zero_tb   : STD_LOGIC;

    -- Helper procedure for printing test results
    procedure print_test_case(
        test_name: string;
        A, B: STD_LOGIC_VECTOR(7 downto 0);
        sel: STD_LOGIC_VECTOR(2 downto 0);
        result: STD_LOGIC_VECTOR(7 downto 0)) is
    begin
        report "Test: " & test_name &

```

```

        " | A=" & integer'image(to_integer(unsigned(A))) &
        " | B=" & integer'image(to_integer(unsigned(B))) &
        " | Result=" & integer'image(to_integer(unsigned(result)))
end procedure;

begin
    -- Unit Under Test (UUT)
    UUT: ALU port map (
        A => A_tb,
        B => B_tb,
        sel => sel_tb,
        Result => Result_tb,
        Zero => Zero_tb
    );

    -- Stimulus Process
    stim_proc: process
    begin
        -- Wait for 10ns for global reset
        wait for 10 ns;

        -- Test Case 1: Addition (000)
        A_tb <= "00000101"; -- 5
        B_tb <= "00000011"; -- 3
        sel_tb <= "000"; -- ADD
        wait for 10 ns;
        print_test_case("Addition", A_tb, B_tb, sel_tb, Result_tb);
        wait for 3 fs;

        -- Test Case 2: Subtraction (001)
        A_tb <= "00001000"; -- 8
        B_tb <= "00000011"; -- 3
        sel_tb <= "001"; -- SUB
        wait for 10 ns;
        print_test_case("Subtraction", A_tb, B_tb, sel_tb, Result_tb);
        wait for 3 fs;

        -- Test Case 3: AND (010)
        A_tb <= "11110000";
        B_tb <= "00001111";
        sel_tb <= "010"; -- AND
        wait for 10 ns;
        print_test_case("AND", A_tb, B_tb, sel_tb, Result_tb);
        wait for 3 fs;
    end
end

```

```

-- Test Case 4: OR (011)
A_tb <= "11110000";
B_tb <= "00001111";
sel_tb <= "011";      -- OR
wait for 10 ns;
print_test_case("OR", A_tb, B_tb, sel_tb, Result_tb);
wait for 3 fs;

-- Test Case 5: XOR (100)
A_tb <= "11110000";
B_tb <= "00001111";
sel_tb <= "100";      -- XOR
wait for 10 ns;
print_test_case("XOR", A_tb, B_tb, sel_tb, Result_tb);
wait for 3 fs;

-- Test Case 6: NOR (101)
A_tb <= "11110000";
B_tb <= "00001111";
sel_tb <= "101";      -- NOR
wait for 10 ns;
print_test_case("NOR", A_tb, B_tb, sel_tb, Result_tb);
wait for 3 fs;

-- Test Case 7: Zero flag test
A_tb <= "00000000";
B_tb <= "00000000";
sel_tb <= "000";      -- ADD
wait for 10 ns;
print_test_case("Zero Flag", A_tb, B_tb, sel_tb, Result_tb);
wait for 3 fs;

-- Test Case 8: Carry operation
A_tb <= "11111111";
B_tb <= "11111111";
sel_tb <= "111";      -- Carry operation
wait for 10 ns;
print_test_case("Carry Op", A_tb, B_tb, sel_tb, Result_tb);
wait for 3 fs;

-- End simulation
report "Simulation completed successfully";
wait;
end process;

```

```
end Behavioral;
```

Processor_tb.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Processor_tb is
end Processor_tb;

architecture Behavioral of Processor_tb is
    -- Component Declaration
    component Processor
        Port (
            clk : in STD_LOGIC;
            reset : in STD_LOGIC;
            instr_addr : out STD_LOGIC_VECTOR (7 downto 0);
            instr : in STD_LOGIC_VECTOR (31 downto 0);
            data_addr : out STD_LOGIC_VECTOR (7 downto 0);
            data_in : out STD_LOGIC_VECTOR (7 downto 0);
            data_out : in STD_LOGIC_VECTOR (7 downto 0);
            data_wr : out STD_LOGIC
        );
    end component;

    -- Test Signals
    signal clk : STD_LOGIC := '0';
    signal reset : STD_LOGIC := '0';
    signal instr_addr : STD_LOGIC_VECTOR (7 downto 0);
    signal instr : STD_LOGIC_VECTOR (31 downto 0);
    signal data_addr : STD_LOGIC_VECTOR (7 downto 0);
    signal data_in : STD_LOGIC_VECTOR (7 downto 0);
    signal data_out : STD_LOGIC_VECTOR (7 downto 0);
    signal data_wr : STD_LOGIC;

    -- Clock period definition
    constant CLK_PERIOD : time := 10 ns;

begin
    -- Instantiate the Unit Under Test (UUT)
    UUT: Processor port map (
        clk => clk,
        reset => reset,
```



```

    instr_addr => instr_addr,
    instr => instr,
    data_addr => data_addr,
    data_in => data_in,
    data_out => data_out,
    data_wr => data_wr
);

-- Clock process
clk_process: process
begin
    clk <= '0';
    wait for CLK_PERIOD/2;
    clk <= '1';
    wait for CLK_PERIOD/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- Initialize
    reset <= '1';
    data_out <= x"00";
    wait for CLK_PERIOD*2;

    -- Release reset
    reset <= '0';
    wait for CLK_PERIOD;

    -- Test ADD instruction
    instr <= "00000000" & x"FF" & x"01" & x"00"; -- ADD FF + 01
    wait for CLK_PERIOD;

    -- Test SUB instruction
    instr <= "00100000" & x"FF" & x"01" & x"00"; -- SUB FF - 01
    wait for CLK_PERIOD;

    -- Test AND instruction
    instr <= "01000000" & x"FF" & x"0F" & x"00"; -- AND FF & 0F
    wait for CLK_PERIOD;

    -- Test OR instruction
    instr <= "01100000" & x"F0" & x"0F" & x"00"; -- OR F0 | 0F
    wait for CLK_PERIOD;

```

```

-- Test XOR instruction
instr <= "10000000" & x"FF" & x"55" & x"00"; -- XOR FF ^ 55
wait for CLK_PERIOD;

-- Test NOR instruction
instr <= "10100000" & x"FF" & x"00" & x"00"; -- NOR FF NOR 00
wait for CLK_PERIOD;

-- Wait for a few more cycles
wait for CLK_PERIOD*4;

-- Test reset again
reset <= '1';
wait for CLK_PERIOD*2;
reset <= '0';

wait;
end process;
end Behavioral;

```

Top_tb.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Top_tb is
end Top_tb;

architecture Behavioral of Top_tb is
-- Component Declaration
component Top
  Port (
    clk : in STD_LOGIC;
    reset : in STD_LOGIC
  );
end component;

-- Test Signals
signal clk : STD_LOGIC := '0';
signal reset : STD_LOGIC := '0';

-- Clock period definition
constant CLK_PERIOD : time := 10 ns;

```

```

begin
    -- Instantiate the Unit Under Test (UUT)
    UUT: Top port map (
        clk => clk,
        reset => reset
    );

    -- Clock process
    clk_process: process
    begin
        clk <= '0';
        wait for CLK_PERIOD/2;
        clk <= '1';
        wait for CLK_PERIOD/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        -- Initialize with reset
        reset <= '1';
        wait for CLK_PERIOD*4;

        -- Release reset and let it run
        reset <= '0';
        wait for CLK_PERIOD*20;  -- Run for 20 clock cycles

        -- Apply reset again
        reset <= '1';
        wait for CLK_PERIOD*2;
        reset <= '0';

        -- Let it run some more
        wait for CLK_PERIOD*20;

        -- End simulation
        wait;
    end process;
end Behavioral;

```

simulate.sh

```
#!/bin/bash
```

```

# Create work directory if it doesn't exist
mkdir -p work
cd work

# Clean up any existing files
rm -f *.cf *.vcd *.o

# Analysis (compilation) phase
echo "Compiling VHDL files..."
ghdl -a --workdir=. ../src/CustomALU_Pkg.vhd
ghdl -a --workdir=. ../src/ALU.vhd
ghdl -a --workdir=. ../src/InstrMem.vhd
ghdl -a --workdir=. ../src/DataMem.vhd
ghdl -a --workdir=. ../src/Processor.vhd
ghdl -a --workdir=. ../src/Top.vhd
ghdl -a --workdir=. ../tb/Processor_tb.vhd
ghdl -a --workdir=. ../tb/Top_tb.vhd

# Elaborate phase
echo "Elaborating testbenches..."
ghdl -e --workdir=. Processor_tb
ghdl -e --workdir=. Top_tb

# Run simulation and generate VCD file for Processor testbench
echo "Running Processor simulation..."
ghdl -r --workdir=. Processor_tb --vcd=processor_tb.vcd --stop-time=200ns

# Run simulation and generate VCD file for Top testbench
echo "Running Top simulation..."
ghdl -r --workdir=. Top_tb --vcd=top_tb.vcd --stop-time=500ns

echo "Simulation complete. VCD files generated."
echo "To view waveforms, run:"
echo "gtkwave work/processor_tb.vcd"
echo "gtkwave work/top_tb.vcd"

cd ..

```

view_waves.sh

```

#!/bin/bash

# View processor testbench waveform
echo "Opening Processor testbench waveform..."
gtkwave -A work/processor_tb.vcd processor_wave.gtkw &

```

```
# Wait a bit before opening the second window
sleep 1

# View top testbench waveform
echo "Opening Top testbench waveform..."
gtkwave -A work/top_tb.vcd top_wave.gtkw &
```

To compile the processor run :

```
./simulate.sh
```

and to view waves run:

```
./view_waves.sh
```

